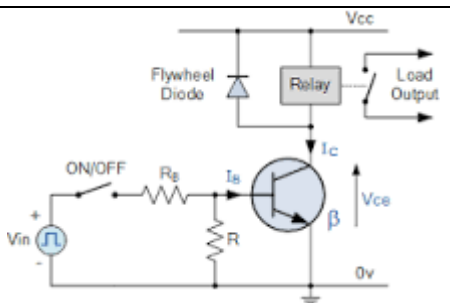


**WEEK ENDING.....14/10/2022.....**


**SUBJECT...INTEGRATED SCIENCE**

**REFERENCE...SYLLABUS(CRDD.2007), SCIENCE FOR JHS .....**

**FORM.....BASIC 8.....WEEK.....5.....**

<b><u>DAY/DURATION</u></b>	<b><u>TOPIC/SUB-TOPIC/ASPECT</u></b>	<b><u>OBJECTIVES/R.P. K</u></b>	<b><u>TEACHER-LEARNER ACTIVITIES</u></b>	<b><u>T/L MATERIALS</u></b>	<b><u>CORE POINTS</u></b>	<b><u>EVALUATION AND REMARKS</u></b>
<b>TUESDAY</b>  <b>11-10-202</b>  <b>1:20PM - 2:40PM</b> <b>80min</b>	<b>Topic;</b> Basic Electronics  <b>Sub-Topic;</b>  Turning on or off of transistors.	By the end of the lesson the Pupil will be able to;  Turn on or off transistors in an electric circuit.  <b>RPK</b> Pupils can identify the various parts of a transistor.	<b>Introduction;</b> Engage Pupils to watch a video play of how to on and off a transistor in a circuit.  <b>Activities;</b> <ol style="list-style-type: none"> <li>1. Demonstrate how to turn on or off of a transistor for Pupils to observe.</li> <li>2. Pupils in small groups to practice turning on or off of transistors.</li> </ol> <b>Closure</b> Through questions and answers, conclude the lesson.	<b>Battery, Switch, led bulb, Wire, Pictures.</b>	 <p>With a zero signal applied to the Base of the transistor it turns "OFF" acting like an open switch and zero collector current flows. With a positive signal applied to the Base of the transistor it turns "ON" acting like a closed switch and maximum circuit current flows through the device.</p>	<b>Exercise;</b> Explain the steps to follow to turn on or off a transistor in a circuit.

## Push Button ON OFF Switch

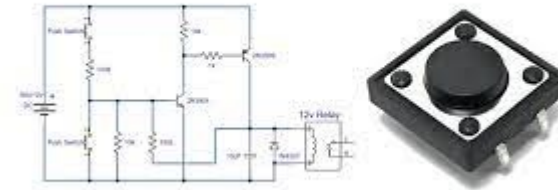

CIRCUITS BY

### Advantages of transistor:

- It is used for fast switching applications.
- Smaller mechanical sensitivity.
- It is used as a current controlled current gain.
- It is available at very low cost.
- It is very smaller in size.
- Fast switching.
- It has a longer life
- Low operating voltage for greater safety
- lower costs
- tighter clearances.

### Disadvantages of transistors;

1. It has reverse blocking capacity is very low.
2. It can be damaged due to the thermal runaway or second breakdown
3. . Manufacturing techniques are very complex and require a clean room environment.

### Exercise;

- 1.State and explain 3 advantages of a transistor.
2. Explain 2 disadvantages of using transistors in circuits.

### REMARKS

**THURSDAY**

**13-10-2022**

**8:05AM – 9:15AM  
70min**

### Topic;

Basic Electronics

### Sub-Topic;

Advantages and Disadvantages of using transistors.

### Objective;

By the end of the lesson the Pupil will be able to;

Explain the advantages and disadvantages of using transistors.

### RPK

Pupils were taught lessons on transistors in basic 7.

### Introduction;

Review Pupils knowledge on the previous lesson.

### Activities;

1. Discuss with Pupils the importance of using transistors in circuits.
2. Pupils brainstorm to explain the disadvantages of using transistors in circuits.

### Closure

Through questions and answers, conclude the lesson.

					4. Due to its small size, it is difficult to trace out faulty ones due to failure.	
--	--	--	--	--	--	--